

C16-EC-505

6633

### BOARD DIPLOMA EXAMINATION, (C-16) OCT/NOV—2018 DECE—FIFTH SEMESTER EXAMINATION

INDUSTRIAL ELECTRONICS

Time: 3 hours]

[Total Marks: 80

#### PART—A

 $3 \times 10 = 30$ 

- Instructions: (1) Answer all questions.
  - (2) Each question carries **three** marks.
  - (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
  - **1.** State the principle of induction heating.
  - **2.** Mention the ratings of SCR.
  - **3.** Draw the symbol SCR, LASCR and SCS.
  - **4.** Give the classification of control systems.
  - **5.** State the need of PLC.
  - **6.** Explain Magnetostriction effect.
  - **7.** Define the term Ultrasonic.
  - **8.** State the need of inverters.
  - **9.** List the applications of UPS.
- **10.** List the applications of dielectric heating.

/6633

[Contd...

*Instructions*: (1) Answer *any* **five** questions.

4

- (2) Each questions carries **ten** marks.
- (3) Answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.
- **11.** Explain construction and working of SCR.
- **12.** Explain construction and working of UJT
- **13.** Draw and explain Volt-Ampere characteristics of TRAIC under forward/reverse bias.
- **14.** Explain PWM voltage control of inverter.
- **15.** Explain the contruction and working of pulsed-echo ultrasonic flaw detector.
- **16.** Explain the contruction, working principle and application of resistance strain gauge.
- **17.** Give comparison between open loop and close loop control systems with examples.
- **18.** Explain the basic circuit of AC resistance welding and explain its working.

\* \* \*

/6633

#### 6633 BOARD DIPLOMA EXAMINATION MARCH/APRIL - 2019 DIPLOMA IN ELECTRONICS AND COMMUNICATION ENGINEERING INDUSTRIAL ELECTRONICS FIFTH SEMESTER EXAMINATION

**Time: 3 Hours** 

**Total Marks: 80** 

**PART - A**  $(3m \times 10 = 30m)$ 

Note 1:Answer all questions and each question carries 3 marks 2:Answers should be brief and straight to the point and shall not exceed 5 simple sentences

- 1. List the applications of DIAC and TRIAC
- <sup>2</sup>. Draw the equivalent circuit of UJT?
- 3. What is the need of Uninterrupted Power Supply?
- 4. What is the need of inverter?
- 5. Classify transducers on the basis of principle of operation and applications
- 6. Write any three applications of LVDT
- 7. What is the meaning of skin effect?
- 8. Write any three advantages of resistance welding?
- 9. What is the need for PLC?
- 10. What is the meaning of actuating signal in control system?

#### **PART - B** $(10m \ x \ 5 = 50m)$

Note 1:Answer any five questions and each carries 10 marks

2: The answers should be comprehensive and the criteria for valuation is the content but not the length of the answer

- 11. Explain the construction and working of Uni Junction Transistor?
- 12. Explain SCR triggering using ?UJT
- 13. Explain the construction and working of GTO SCR?
- 14. Explain the working of Online UPS and Offline UPS.
- 15. Explain the construction and working of piezoelectric ultrasonic generator?

WWW.MANARESULTS.CO.IN

16. Explain the working of Accelerometer?

\*

\*

- 17. Explain about HF power soruce for induction heating.
- 18. Explain an open loop control system with any two examples

- xxx -

# WWW.MANARESULTS.CO.IN

#### 6633 BOARD DIPLOMA EXAMINATION JUNE - 2019 DIPLOMA IN ELECTRONICS AND COMMUNICATION ENGINEERING INDUSTRIAL ELECTRONICS FIFTH SEMESTER EXAMINATION

**Time: 3 Hours** 

**Total Marks: 80** 

**PART - A**  $(3m \times 10 = 30m)$ 

Note 1:Answer all questions and each question carries 3 marks 2:Answers should be brief and straight to the point and shall not exceed 5 simple sentences

- 1. Draw the circuit symbols of GTOSCR, SUS, SCS?
- 2. Define intrinsic stand-off ratio of UJT.
- 3. Write any 3 applications of UPS?
- 4. Draw the output voltage waveforms of Sinusoidal pulse width modulation inverter?
- 5. Explain magnetostriction effect.
- 6. Write any three disadvantages of LVDT?
- 7. What is the principle of induction heating?
- 8. Draw the block diagram of a resistance welding system that uses sequence timer
- 9. Write any three features of open loop control system?
- 10. Define transfer function.

#### **PART - B** $(10m \ x \ 5 = 50m)$

Note 1:Answer any five questions and each carries 10 marks 2:The answers should be comprehensive and the criteria for valuation is the content but not the length of the answer

- 11. Explain about construction and working of Uni Junction Transistor?
- 12. Explain the working of SCR using two transistor analogy?
- 13. Explain about the speed control of D.C Motor using single Phase half wave SCR rectifier?
- 14. Explain the working of MOSFET based Inverter circuit?
- 15. Explain the construction and working of LVDT? WWW.Manalesuits.co.in

- 16. Explain the construction and working of magnetostriction oscillator and how ultrasonics are generated?
- 17. Explain the basic circuit of AC resistance welding and explain its working?
- 18. Explain an closed loop control system with any two examples

\*

\*

- xxx -

# C16-EC-505

## 6633

#### **BOARD DIPLOMA EXAMINATIONS**

#### **OCT/NOV-2019**

#### **DECE-FIFTH SEMESTER**

#### INDUSTRIAL ELECTRONICS

Time:3 hours

#### Max. Marks: 80

#### PART – A

#### $3 \ge 10 = 30$

- Instructions: 1. Answer all questions.
  - 2. Each question carries Three Marks.
  - 3. Answer should be brief and straight to the point and should not exceed five simple sentences.
- 1. Draw the V-I characteristics of DIAC.
- 2. Compare GTOSCR and SCR.
- 3. List the applications of inverters.
- 4. State the advantages of SMPS.
- 5. Classify electronic transducers based on principle of operation.
- 6. State the working principle of strain gauge.
- 7. List the applications of induction heating.
- 8. Classify Different Types of ELECTRICAL WELDING.
- 9. Define transfer function.
- 10. List the applications of PLCs.

[cont...

Instructions: 1. Answer any Five questions

- 2. Each question carries **TEN** Marks.
- 3. Answer should be comprehensive and Criteria forValuation is the content but not the length of the answer.
- 11. Explain the construction and working of SCR with a sketch.
- 12. Draw and explain the V-I characteristics of TRIAC with its constructional details.
- 13. Explain the triggering of SCR using UJT with a diagram.
- 14. Explain the working of off-line UPS with a diagram.
- 15. Explain the construction and working of LVDT.

\*

- 16. Explain the construction and working of Thermo-Couple Transducer.
- 17. a) Compare induction heating and dielectric heating. 4M

b) Explain the principle of resistance welding with a sketch. 6M

18. Draw the Block diagram of Closed Loop System and Explain.



с16-ес-505

## 6633

# BOARD DIPLOMA EXAMINATION, (C-16) NOVEMBER-2020

**DECE—FIFTH SEMESTER EXAMINATION** 

INDUSTRIAL ELECTRONICS

Time : 3 hours ]

[ Total Marks : 80

#### PART—A

3×10=30

Instructions: (1) Answer all questions.

- (2) Each question carries **three** marks.
- (3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.
- 1. Define intrinsic stand-off ratio of UJT.
- **2**. List the applications of SCR.
- **3**. List the application of inverters.
- 4. List the applications of SMPS.
- **5**. Classify electrical transducers on the basis of principle of operation and applications.
- **6**. List applications of resistance strain guage.
- 7. Classify industrial heating methods.
- 8. List the applications of dielectric heating.
- 9. Define transfer function of control system.
- **10**. State the need for PLC.

/6633

[ Contd....

*Instructions* : (1) Answer *any* **five** questions.

\*

- (2) Each question carries **ten** marks.
- (3) Answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.
- **11**. Explain the construction and working of GTO SCR.
- **12**. Explain the construction and working of TRIAC with its volt ampere characteristics.
- 13. Explain the speed control of DC motor using SCR.
- 14. Explain the working of SMPS with the block diagram.
- **15**. Explain the construction and working of Piezo-electric transducer.
- **16**. Explain construction and working of Pulsed-echo ultrasonic flaw detector.
- **17**. Explain about the electrodes used in dielectric heating and method of coupling to RF generator.
- **18**. Draw and explain the block diagram of a closed loop control system and describe with an example.

 $\star \star \star$ 

/6633

\*

2

AA20—PDF

#### 

C16-EC-505

### 6633

#### BOARD DIPLOMA EXAMINATION, (C-16)

#### MARCH/APRIL-2021

#### DECE - FIFTH SEMESTER EXAMINATION

#### INDUSTRIAL ELECTRONICS

Time: 3 hours ]

[ Total Marks : 80

3×10=30

#### PART—A

**Instructions**: (1) Answer **all** questions.

- (2) Each question carries three marks.
- (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.
- **1.** List any six different thyristor family devices.
- 2. Distinguish among SVS, SBS and SCS.
- **3.** List the applications of SMPS.
- 4. Explain the working principle of inverter.
- 5. Classify transducers based on principle of operation.
- 6. Explain piezoelectric effect.
- 7. List applications of dielectrical heating.
- 8. Classify industrial heating methods.
- 9. Define transfer function.
- **10.** Give any three examples of closed loop control system.

/6633

[Contd...

PART—B

**Instructions :** (1) Answer *any* **five** questions.

\*

- (2) Each question carries ten marks.
- (3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.
- **11.** Explain the construction and working of SCR with a neat sketch.
- **12.** Explain construction and working of UJT.
- **13.** Explain different triggering modes of TRIAC with neat diagrams.
- **14.** Explain the working of ON-LINE UPS with neat diagram.
- **15.** Explain the constructional details and working principle of strain gauge.
- **16.** Explain the construction and working of magnetostriction oscillator and explain how ultrasonics are generated.
- **17.** Draw and explain basic circuit for AC resistance welding.
- **18.** Explain PLC system with a block diagram.

 $\star \star \star$